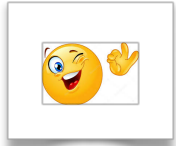




ELECTRIC CIRCUIT

A) Write one word that each of the following describes. Guess what they are !



1. When this is closed , the lamp lights up. _____
2. They are microscopic particles. _____
3. There are two of them in a cell; positive and negative. _____
4. It stores chemical energy and transfers it to electrical energy. _____
5. It has a cell, a lamp and a switch. _____
6. It is used to connect the components of a simple circuit. _____
7. It lights up when the switch is closed. _____

B) Write the names of the components used in this simple circuit.

