




Date: Wednesday, 8th April, 2020

ANSWER SHEET

ELECTRIC CIRCUIT

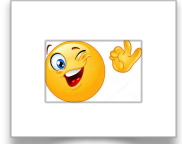A) Write one word that each of the following describes. Guess what they are !



1. When this is closed ,the lamp lights up. **SWITCH**
2. They are microscopic particles. **ELECTRONS**
3. There are two of them in a cell; positive and negative. **TERMINALS**
4. It stores chemical energy and transfers it to electrical energy. **CELL**
5. It has a cell, a lamp and a switch. **SIMPLE CIRCUIT**
6. It is used to connect the components of a simple circuit. **WIRE**
7. It lights up when the switch is closed. **LAMP**

B) Write the names of the components used in this simple circuit.

