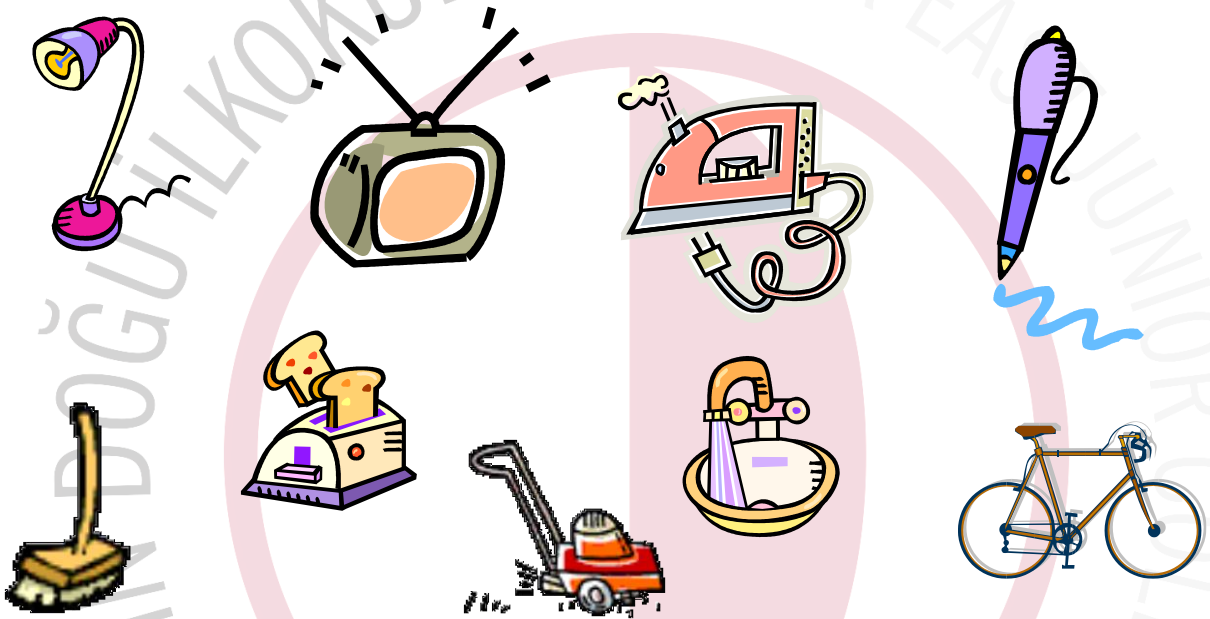




Date: Friday, 10th April, 2020

Unit 5 - ELECTRICITY

A. Please put the pictures in the correct box.




Uses electricity

Doesn't use electricity


B. Match the words with the pictures.



sockets

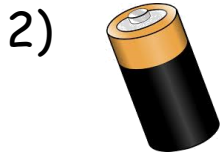

wire

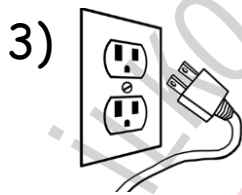

bulb




circuit




battery

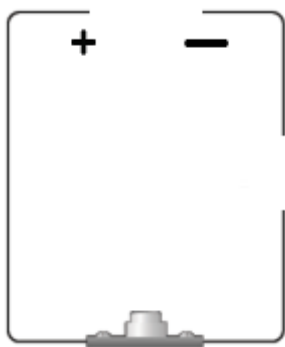C. Use the symbols in the box and complete the circuits.



The switch is ON

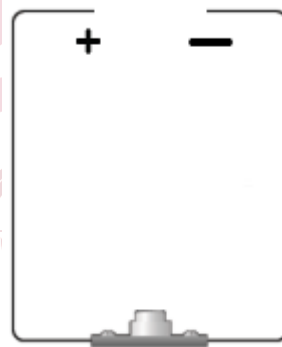

The switch is OFF

